

CCSYA

The Processor

Single-cycle Implementation

Part 1

Departamento de Engenharia Informática
Instituto Superior de Engenharia do Porto

Luís Nogueira (lmn@isep.ipp.pt)

Introduction

- **CPU performance factors**
 - Instruction count - Determined by ISA and compiler
 - CPI and Cycle time - Determined by CPU hardware
- **We will examine two MIPS implementations**
 - A simplified version
 - A more realistic pipelined version (next lectures)
- **Simple subset (shows most aspects)**
 - Memory reference: `lw, sw`
 - Arithmetic/logical: `add, sub, and, or, slt`
 - Control transfer: `beq, j`

Introduction

- **In examining the implementation, we will have the opportunity to see:**
 - How the ISA determines many aspects of the implementation
 - How the choice of various implementation strategies affects the clock rate and CPI
 - How many of the key design principles, such as *Simplicity favors regularity*, can be illustrated
- **In addition, most concepts used to implement the MIPS subset are used to construct a broad spectrum of computers**
 - From high-performance servers to general-purpose microprocessors to embedded processors

Logic Design Conventions

- **To discuss the design of a computer, we must decide:**
 - How the hardware logic implementing the computer will operate
 - How the computer is clocked
- **The datapath elements in the MIPS implementation consist of two different types of logic elements:**
 - Elements that operate on data values (combinational)
 - Elements that contain state (sequential)


Logic Design Basics

- **Information encoded in binary**
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- **Combinational element**
 - Operate on data
 - Output is a function of input
- **State (sequential) elements**
 - Store information
 - Output can depend on both the inputs and the value stored in memory, which is called the state of the block

Combinational Elements


■ AND-gate

- $Y = A \& B$

 


■ Adder

- $Y = A + B$

 


■ Multiplexer

- $Y = S ? I1 : I0$

 



■ Arithmetic/Logic Unit

- $Y = F(A, B)$

 


Sequential Elements

  - **Stores data in a circuit**
 - Uses a clock signal to determine when to update the stored value
 - A clock is simply a free-running signal with a fixed cycle time (or clock period)
- **A clocking methodology is designed to make hardware predictable**
 - **Edge-triggered**: update when Clk changes from 0 to 1




Clocking Methodology

 - The clock must have a **long enough period** so that all the signals in the combinational logic block stabilize
 - To ensure that the values written into the state elements on the active clock edge are valid
- This constraint sets a lower bound on the length of the clock period
 - Which must be long enough for all state element inputs to be valid



Building a Datapath

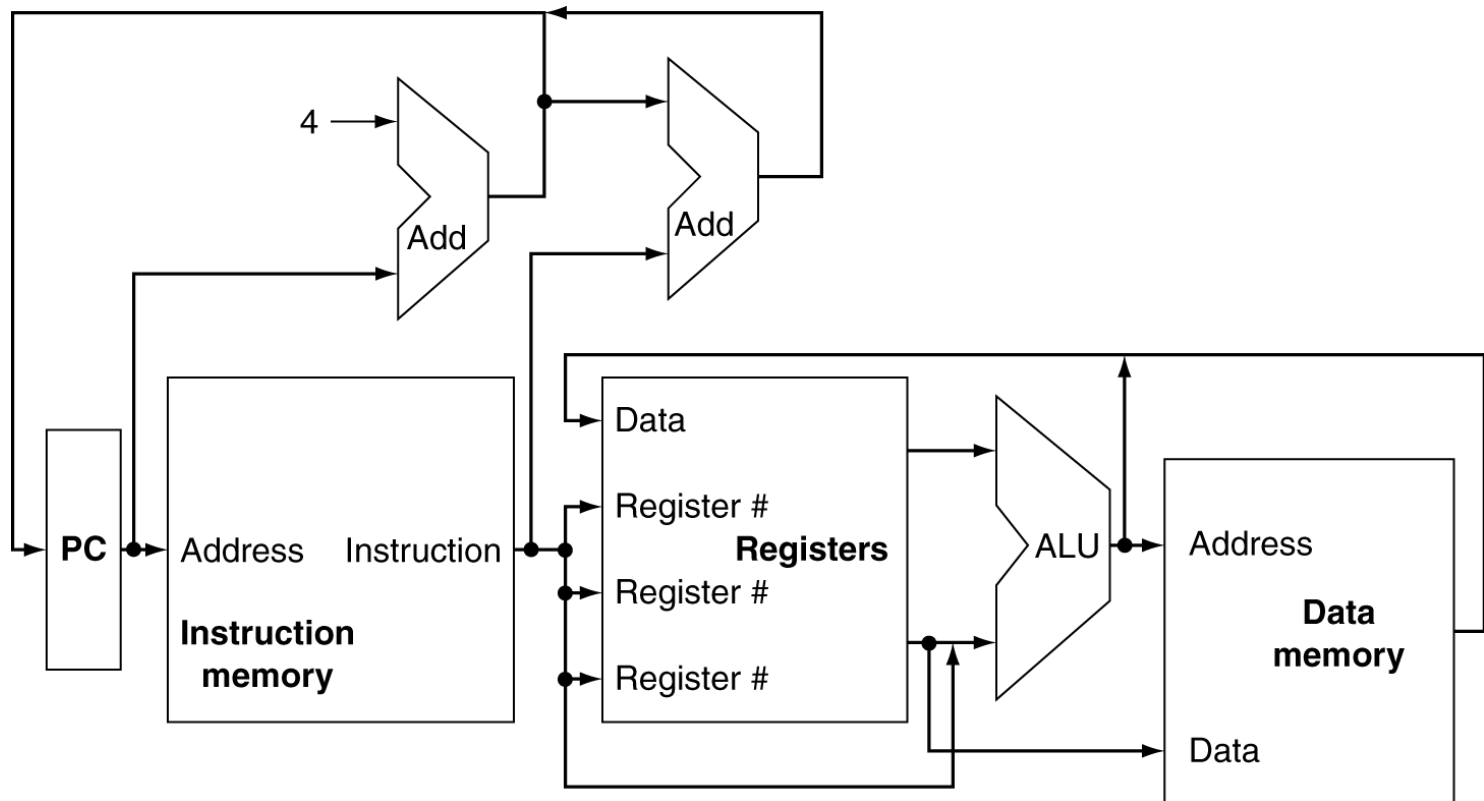
- **Datapath – elements that process data and addresses in the CPU**
 - Registers, ALUs, multiplexers, memories, ...



Datapath – Instruction Fetch

- To execute any instruction, we must start by **fetching the instruction from memory**
- To prepare for executing the next instruction, we must also **increment the program counter**
 - So that it points at the next instruction, 4 bytes later
- **Fetching instructions thus requires:**
 - **Memory unit** where instructions are stored
 - **Program counter**(PC) to hold the address of the current/next instruction
 - **Adder** to increment the PC to the address of the next instruction


Instruction Fetch

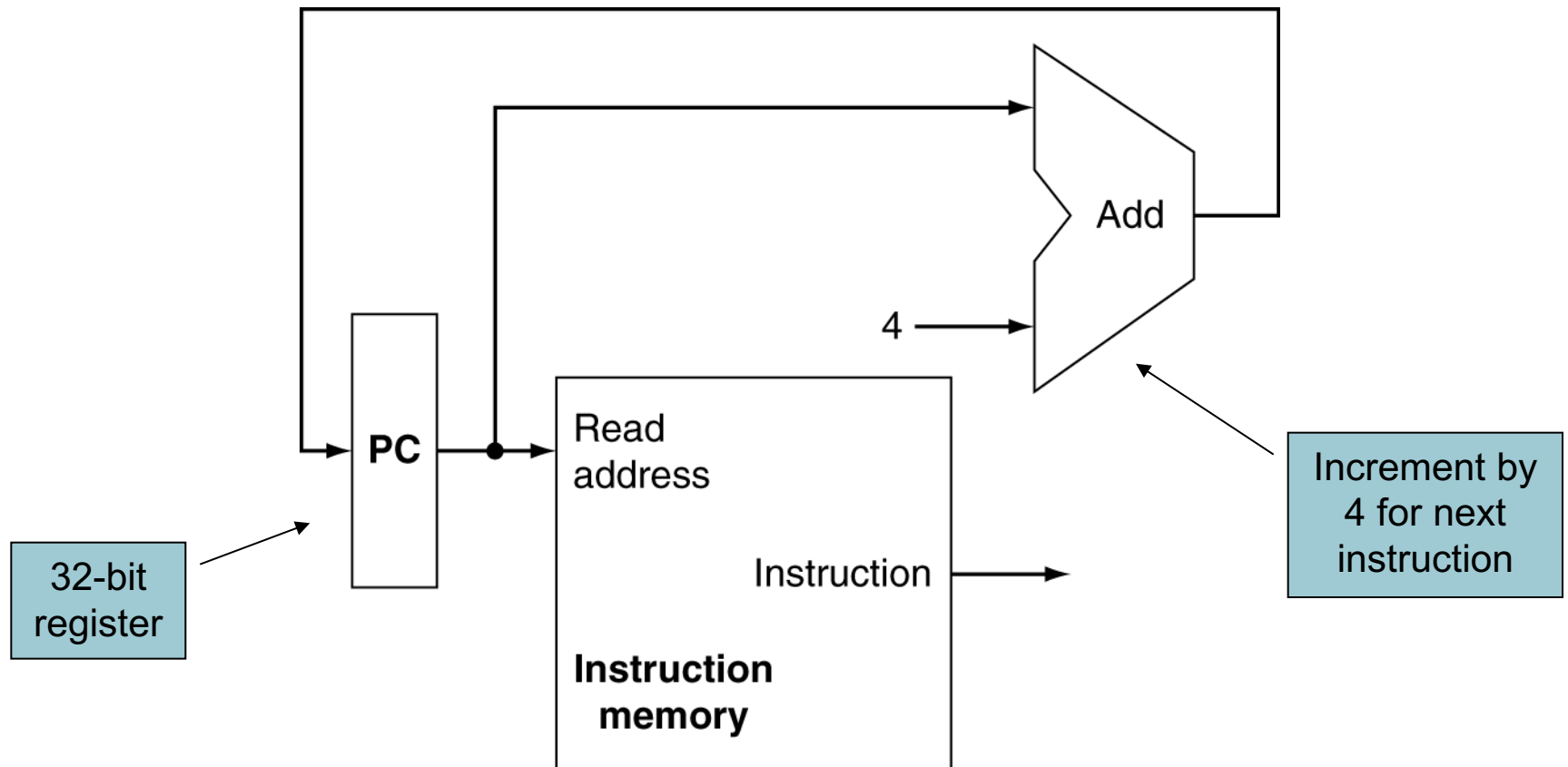


Datapath – R-Type Instructions

- The R-type instructions (e.g., `add $t1, $t2, $t3`) perform arithmetic-logical operations
 - Read two registers
 - Perform an ALU operation on the contents of the registers
 - Write the result to a register
- R-type instructions thus require:
 - **Register file** where the register's contents are stored
 - **ALU** to operate on the values read from the registers

R-Format Instructions

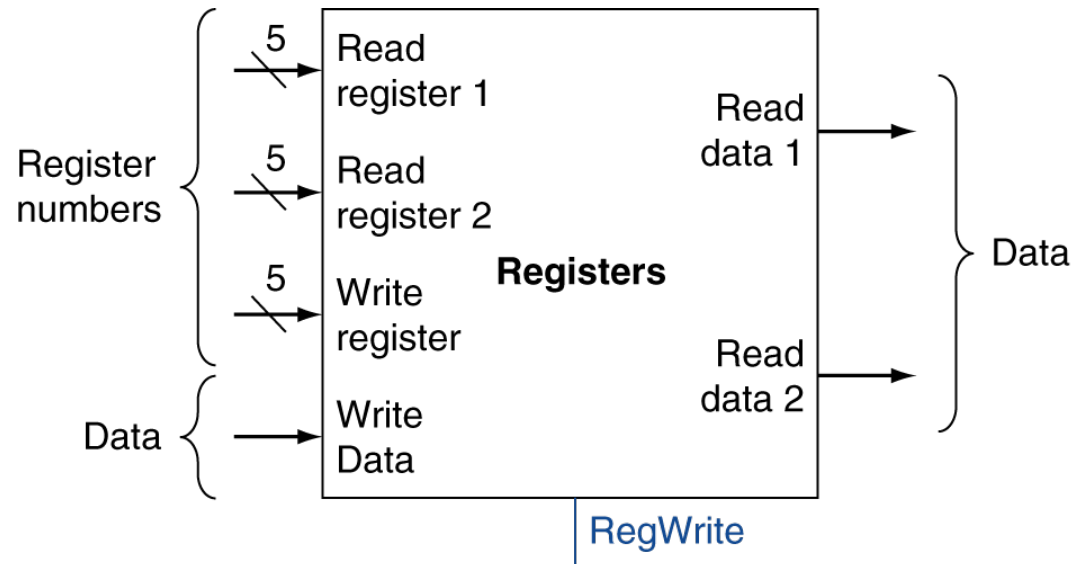

a. Registers

 


b. ALU


Datapath – Load and Store

- **Memory reference instructions (e.g., `lw $t1, offset($t2)`)**
 - Compute a memory address
 - Perform a load or store operation, by adding a base register to a 16-bit signed offset field contained in the instruction
- **Memory reference instructions thus require:**
 - **Register file** where the register's contents are loaded/stored
 - **ALU** to operate on the value read from the base register and the offset
 - **Memory unit** where data is loaded/stored
 - **Sign extension unit** to sign-extend the 16-bit offset field to a 32-bit signed value

Load/Store Instructions

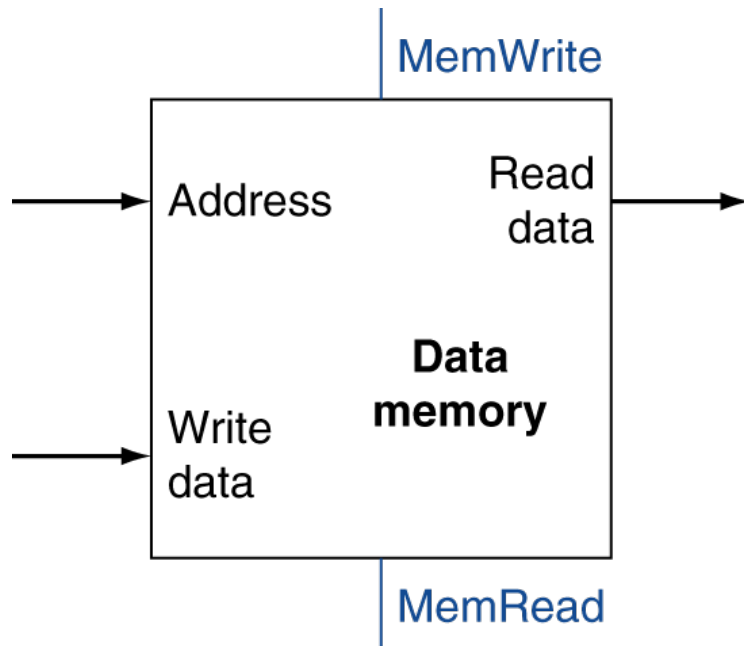

a. Data memory unit

 


b. Sign extension unit

Datapath - Branches

- **Branch instructions (e.g., `beq $t1, $t2, offset`)**
 - Compare two registers
 - Compute a branch target address, by adding the PC+4 (the base for computing the branch target address) to a 16-bit signed offset field contained in the instruction
 - The offset is shifted left 2 bits so that it is a word offset (this shift increases the offset range by a factor of 4)
- **Branch instructions thus require:**
 - **Register file** where the register's contents are stored
 - **ALU** to compare the values read from the registers
 - **Adder** to compute the branch target address
 - **Sign extension** and **shift left units** to sign-extend and shift left the 16-bit offset field to a 32-bit signed value


Branch Instructions

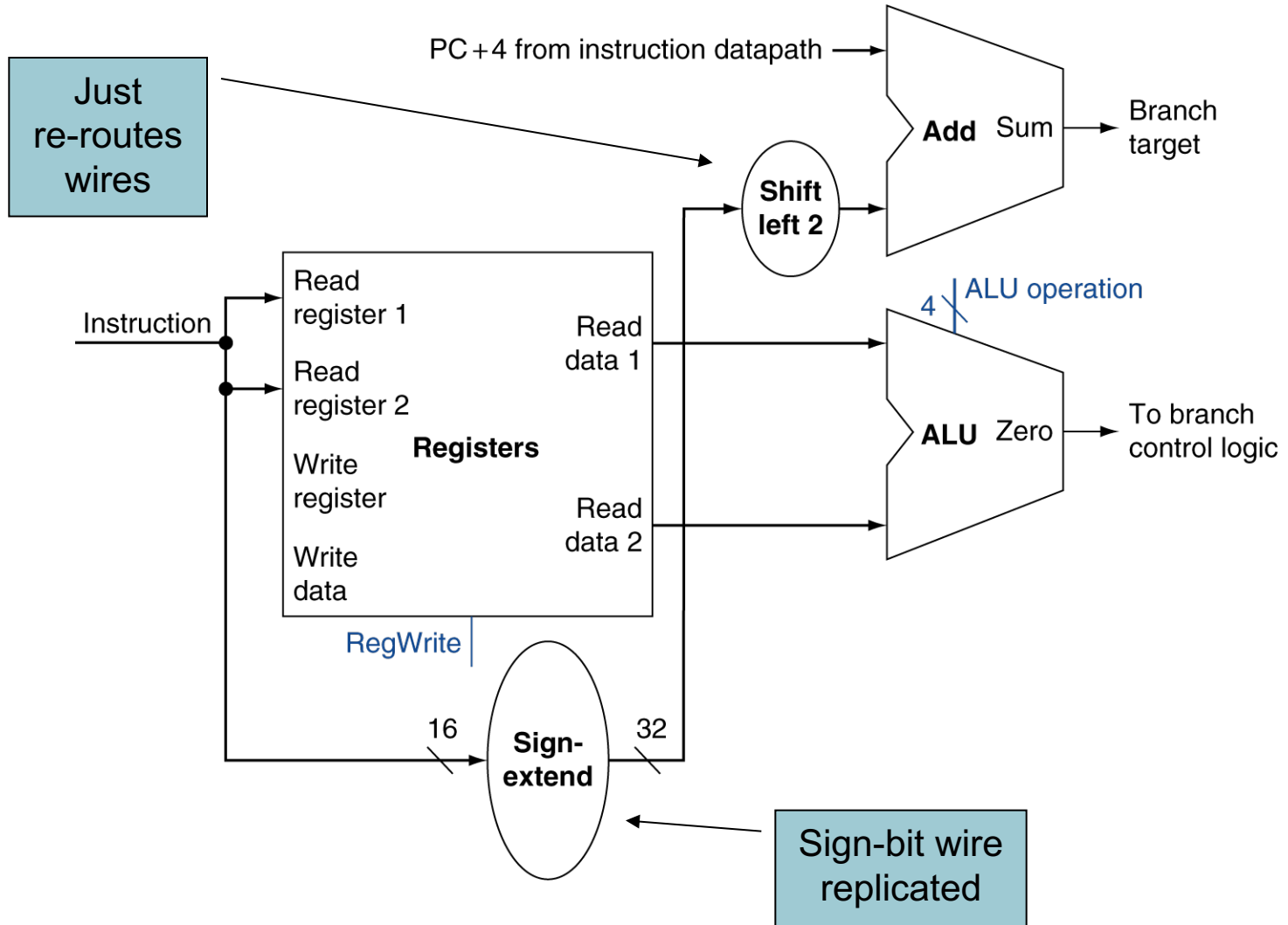

Combining the Elements


- **Our simple datapath executes an instruction in one clock cycle**
 - This means that no datapath resource can be used more than once per instruction, so any element needed more than once must be duplicated
 - Hence, we need **separate instruction and data memories**
- **Although some of the functional units will need to be duplicated, many of the elements can be shared by different instruction flows**
 - Use **multiplexers** and **control signals** where alternate data sources are used for different instructions

Multiplexers

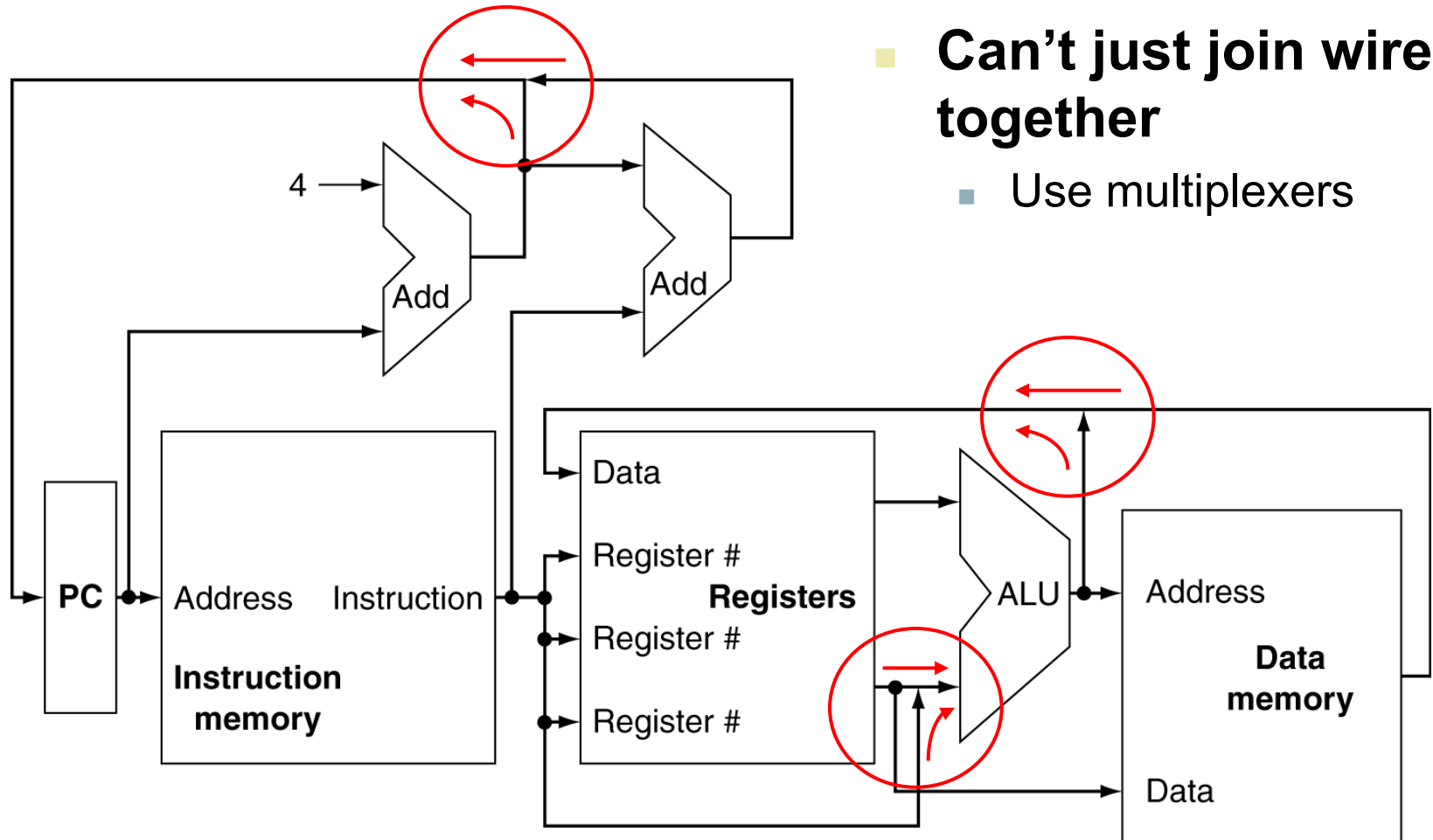

- **Can't just join wires together**
 - Use multiplexers

Datapath – Full Picture

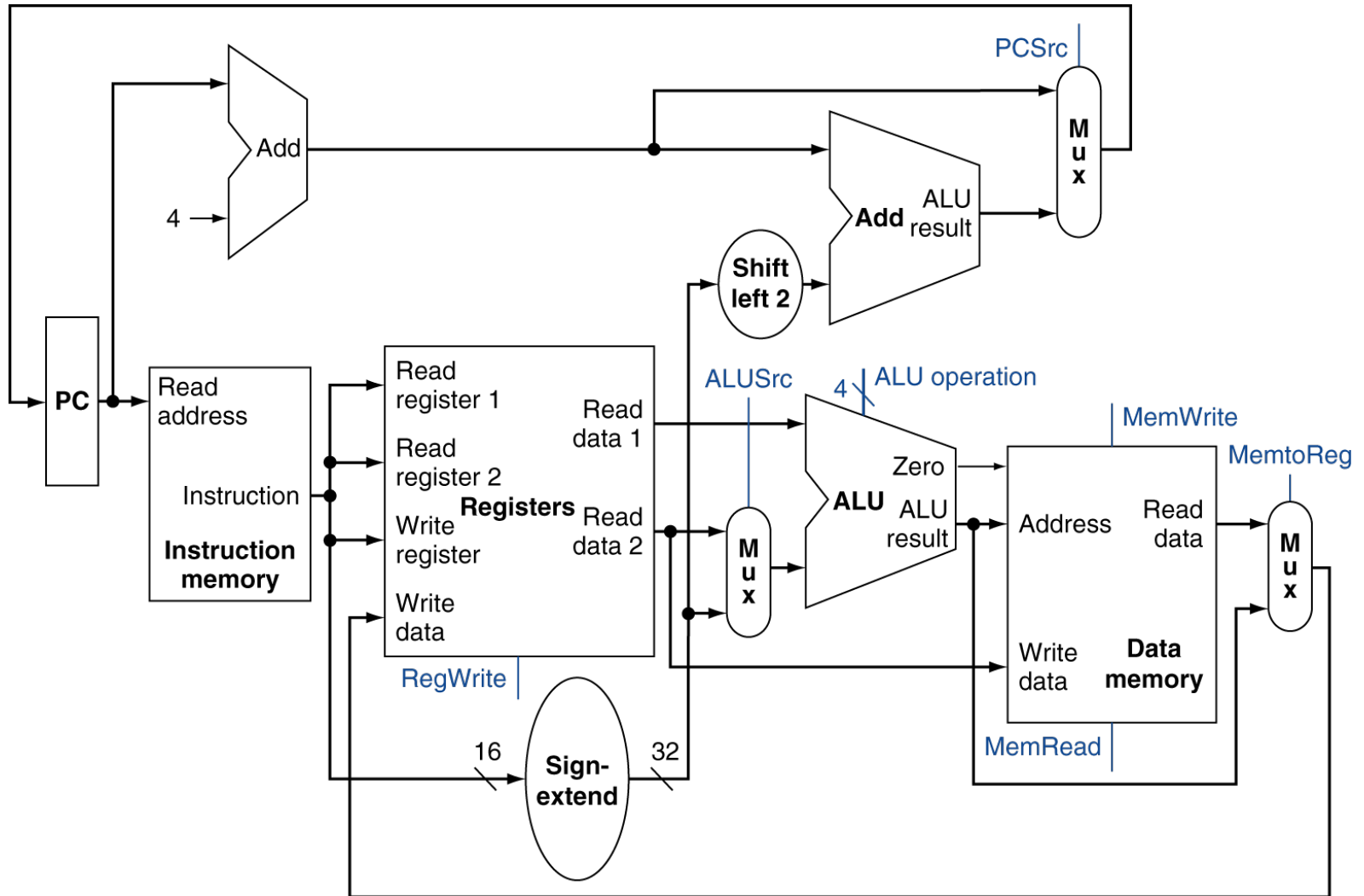

Concluding remarks

- **This datapath can execute the basic instructions in a single clock cycle**
 - (load-store word, ALU operations, and branches)
 - The support for jumps will be added later
- **In the next lecture, we refine this view to fill in the details**
 - Which requires that we add further functional units, increase the number of connections between units, and, of course, a control unit to control what actions are taken for different instruction classes