

**CCSYA**

---


## **The Processor**

### **Pipelining – Part I**

Departamento de Engenharia Informática  
Instituto Superior de Engenharia do Porto

Luís Nogueira ([lmn@isep.ipp.pt](mailto:lmn@isep.ipp.pt))

# Single-cycle Datapath


 


# Pipelining

- **Implementation technique in which multiple instructions are overlapped in execution**
  - Instructions are executed in steps and each step takes one clock cycle
  - Different instructions may take a different number of steps to execute
  - The pipelined clock cycle is determined by the worst-case step
- **Pipelining improves performance by increasing instruction throughput**
  - As opposed to decreasing the average instruction execution time
- **Nearly universal today**
  
# Pipelining Analogy

- **Pipelined laundry: overlapping execution**
  - Parallelism improves performance



- **Four loads:**

- Speedup  
 $= 8/3.5 = 2.3$

- **Non-stop:**

- Speedup  
 $= 2n/0.5n + 1.5 \approx 4$   
 $= \text{number of stages}$


# Pipelining

- Exploits the **potential parallelism among instructions**
  - This parallelism is often called **instruction-level parallelism (ILP)**
- There are two methods for increasing the potential amount of ILP:
  - **Increase the number of steps** (depth) of the pipeline to overlap more instructions (and potentially reduce the clock cycle)
  - **Replicate the functional units** of the computer so that it can launch multiple instructions in every pipeline stage
- In what follows, we will not consider the case of using several functional units per stage

# MIPS Pipeline

- **Five stages, one step per stage**
  1. **IF**: Instruction fetch from memory
  2. **ID**: Instruction decode & register read
  3. **EX**: Execute operation or calculate address
  4. **MEM**: Access memory operand
  5. **WB**: Write result back to register
- **These five steps correspond roughly to the way the data path is drawn**
  - Instructions and data move generally from left to right through the five stages as they complete execution

# MIPS Pipelined Datapath

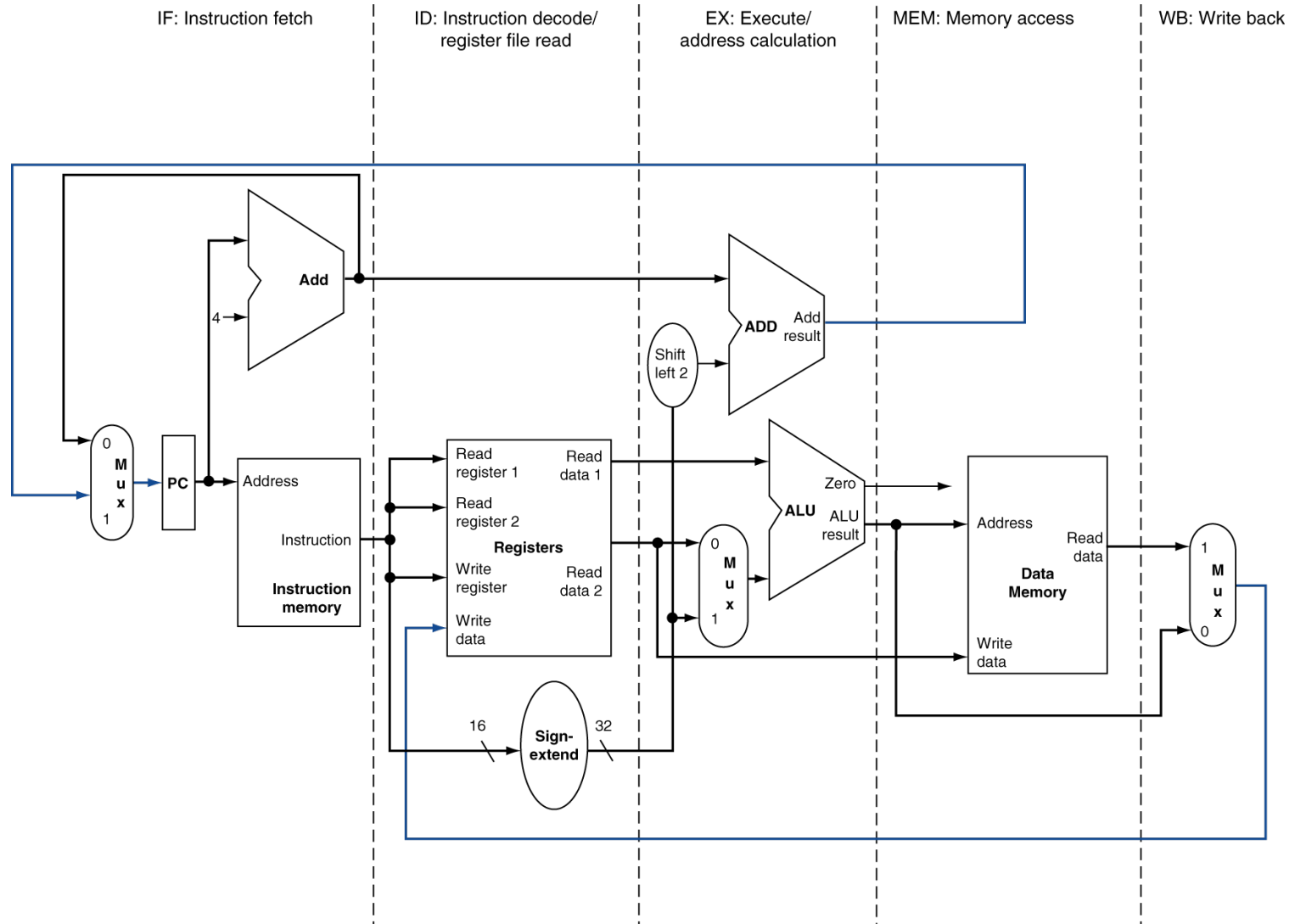



# Pipeline Performance

- **Assume time for stages is**
  - 100ps for register read or write
  - 200ps for other stages
- **Compare pipelined datapath with single-cycle datapath**

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100ps	200ps	200ps	100ps	800ps
sw	200ps	100ps	200ps	200ps		700ps
R-format	200ps	100ps	200ps		100ps	600ps
beq	200ps	100ps	200ps			500ps



# Pipeline Performance

  

# Pipeline Speedup

- **If all stages are balanced (ideal condition)**

- i.e., all take the same time

$$\text{Time between instructions}_{\text{pipelined}} = \frac{\text{Time between instructions}_{\text{nonpipelined}}}{\text{Number of pipe stages}}$$

- **If not balanced, speedup is less**

- Moreover, pipelining involves some overhead, the source of which will be clearer shortly

- **Speedup due to **increased throughput****

- Latency (time for each instruction) does not decrease
- But instruction throughput is the important metric because real programs execute billions of instructions


# Pipelining and ISA Design

- **MIPS ISA designed for pipelining**
- **All instructions are 32-bits**
  - Easier to fetch and decode in one cycle
  - c.f. x86: 1- to 17-byte instructions
- **Few and regular instruction formats**
  - Can decode and read registers in one step
- **Load/store addressing**
  - Can calculate address in 3<sup>rd</sup> stage, access memory in 4<sup>th</sup> stage
- **Alignment of memory operands**
  - Memory access takes only one cycle

# Implementing a Pipelined Datapath

- All instructions advance during each clock cycle from one pipeline stage to the next
- Therefore, we need **pipeline registers** to hold data
  - So that portions of a single datapath can be shared during instruction execution
- The registers are named for the two stages separated by that register
  - IF/ID, ID/EX, EX/MEM, MEM/WB
  - Notice that there is no pipeline register at the end of the write-back stage


# Pipeline registers

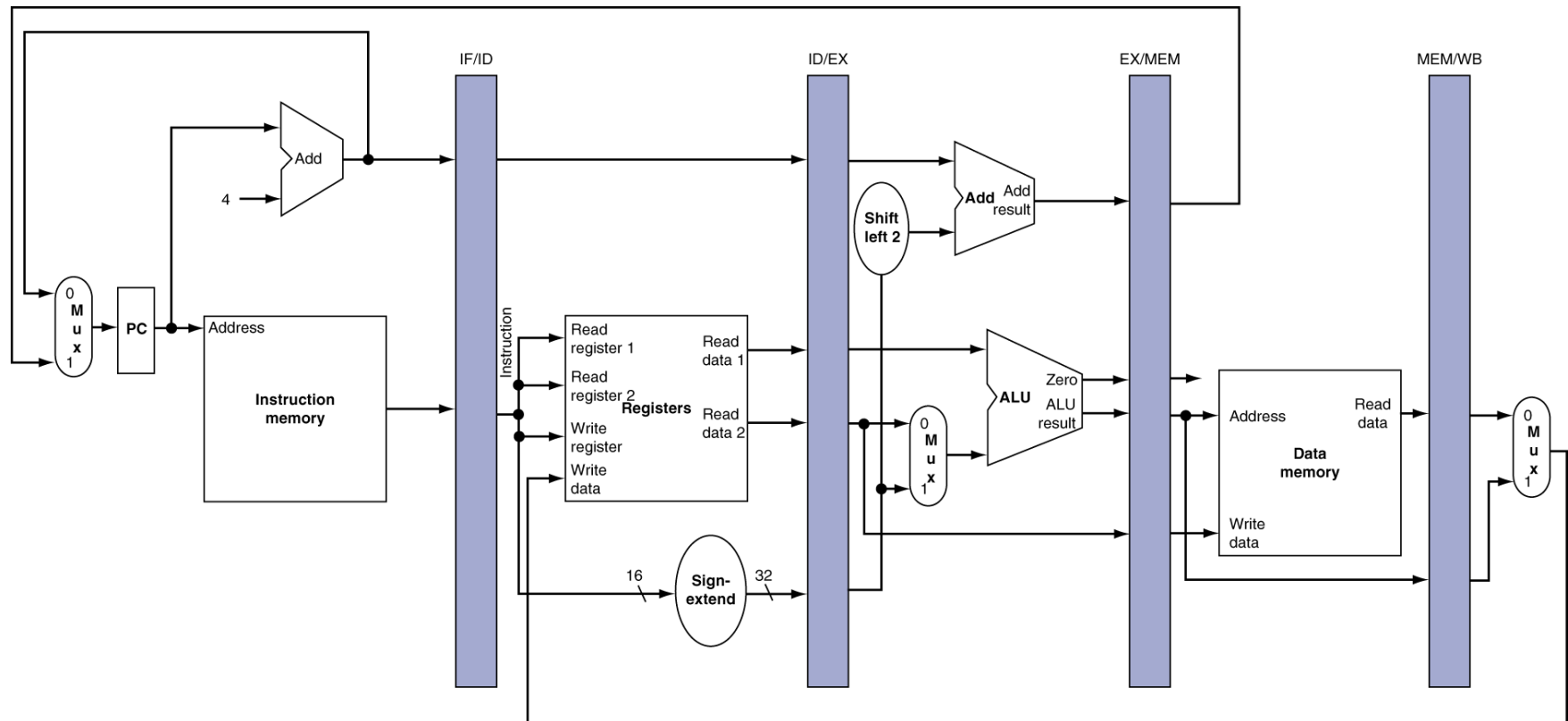


# Pipeline Operation

- **“Single-clock-cycle” pipeline diagram**
  - Shows pipeline usage in a single cycle
  - Highlight the **right half** of registers or memory when they are being **read** and highlight the **left half** when they are being **written**
- **We’ll look at “single-clock-cycle” diagrams for load and store**
  - This walk-through of the load instruction shows that any information needed in a later pipe stage must be passed to that stage via a pipeline register
  - Walking through a store instruction shows the similarity of instruction execution, as well as passing the information for later stages

# IF for Load, Store, ...

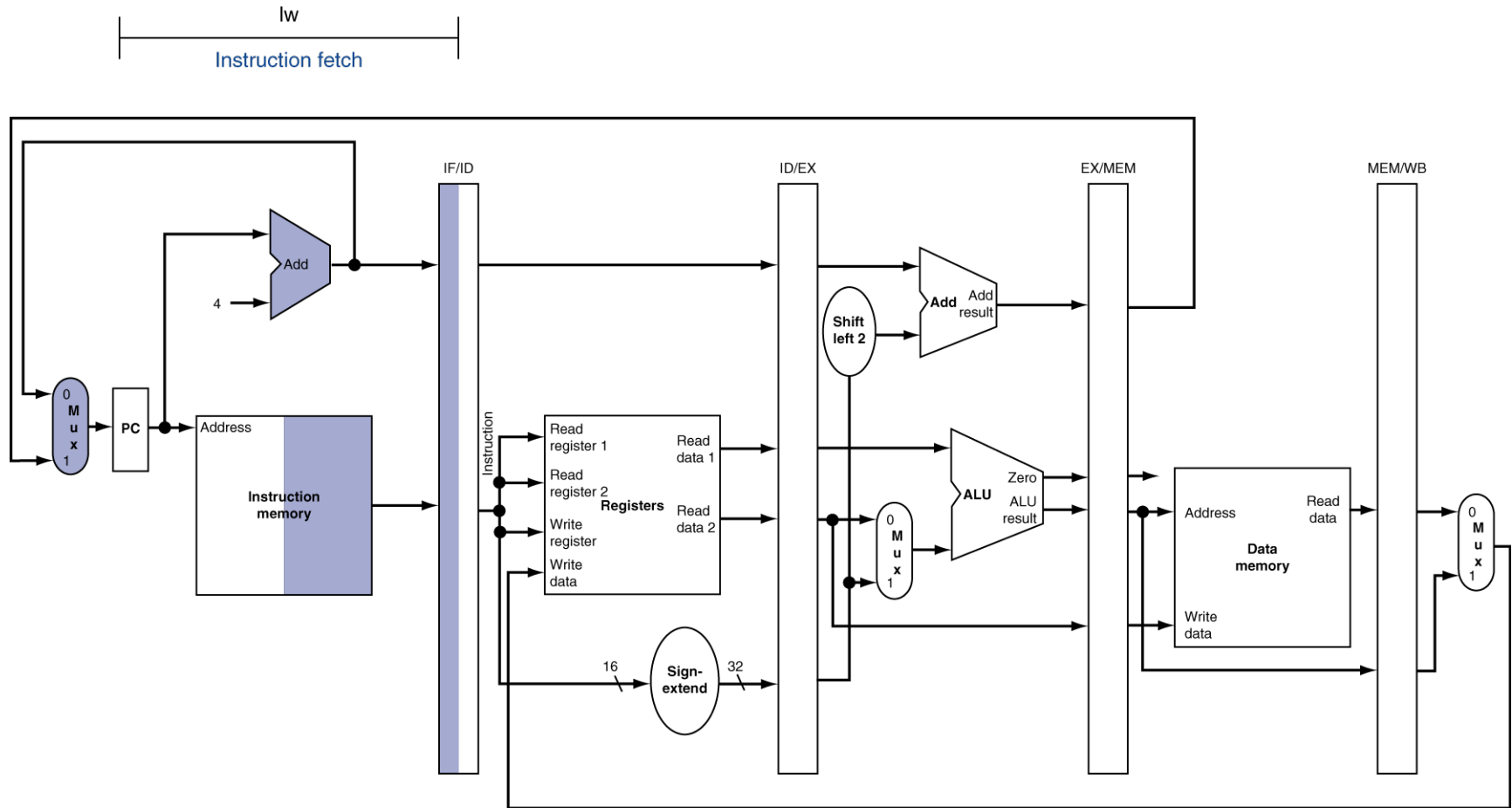


# ID for Load, Store, ...

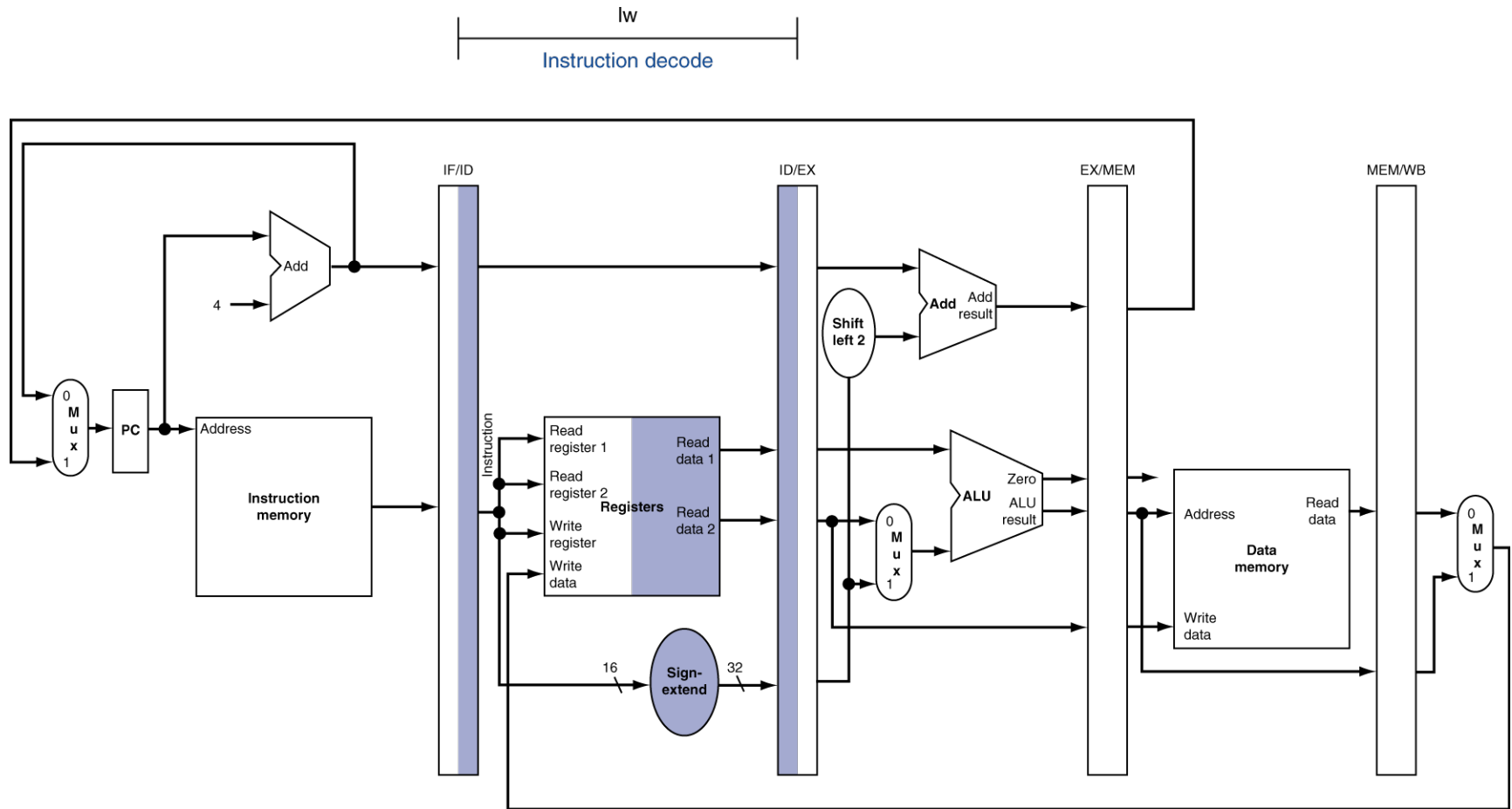





# EX for Load

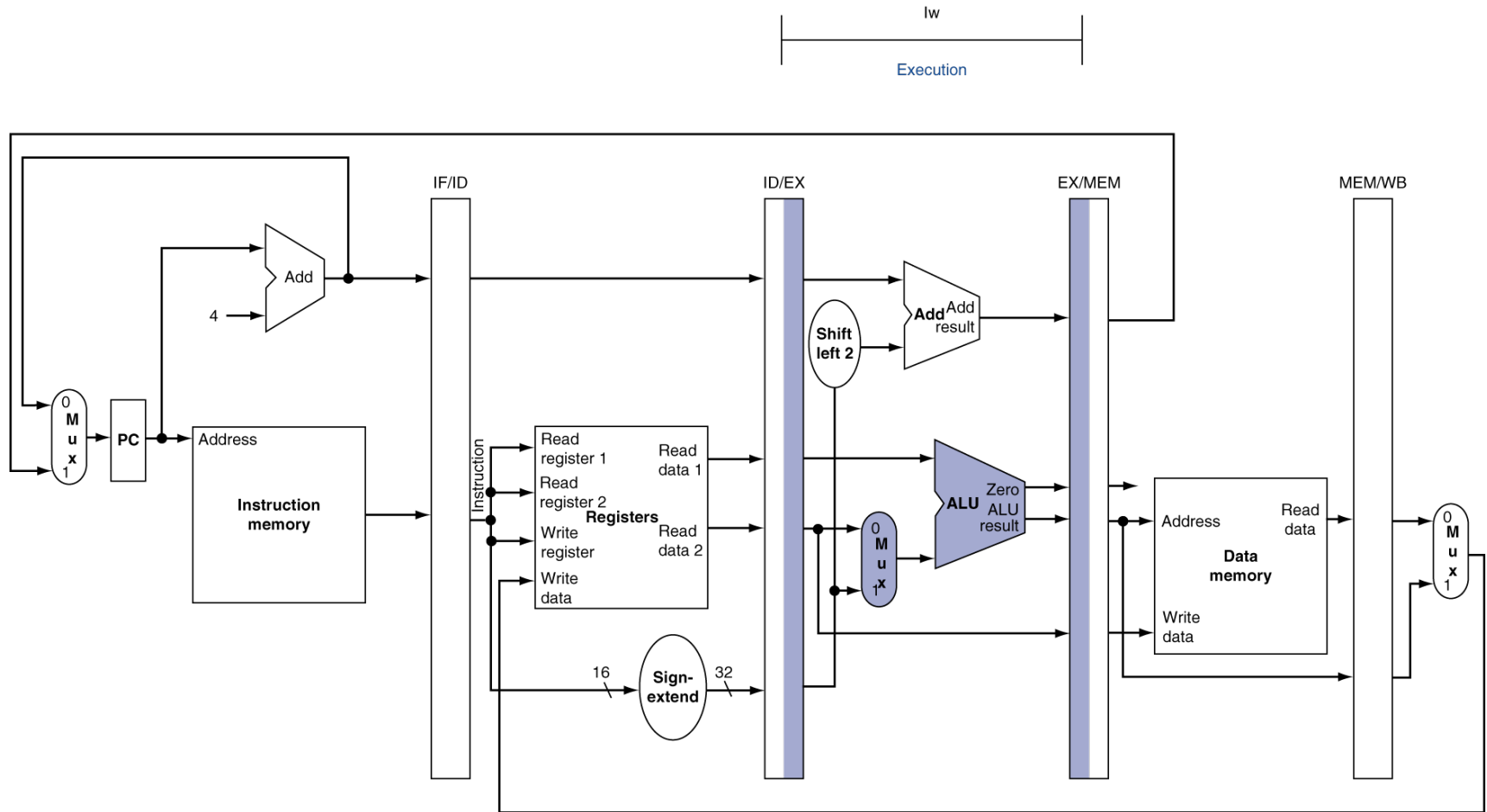


# MEM for Load

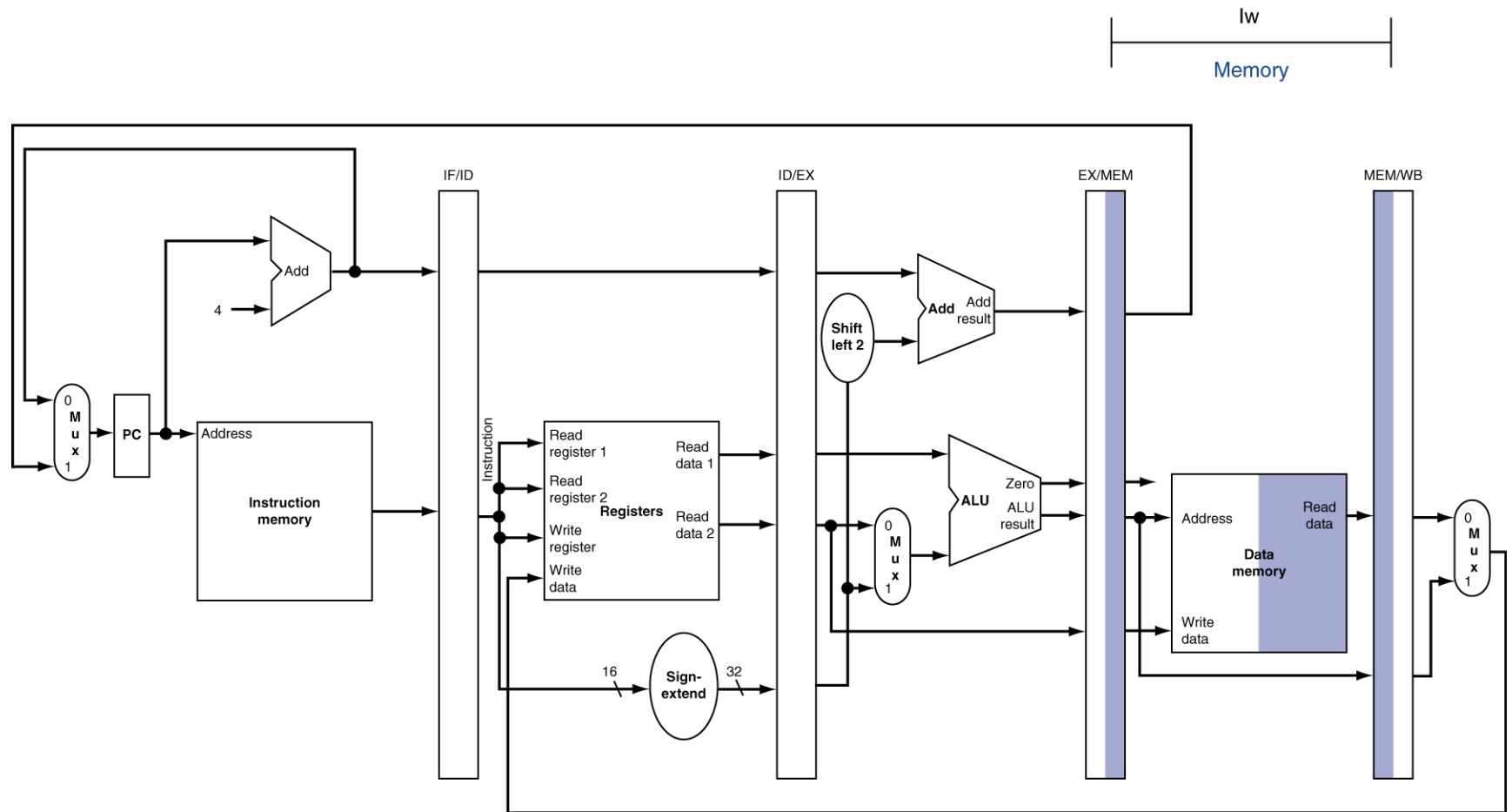

# WB for Load

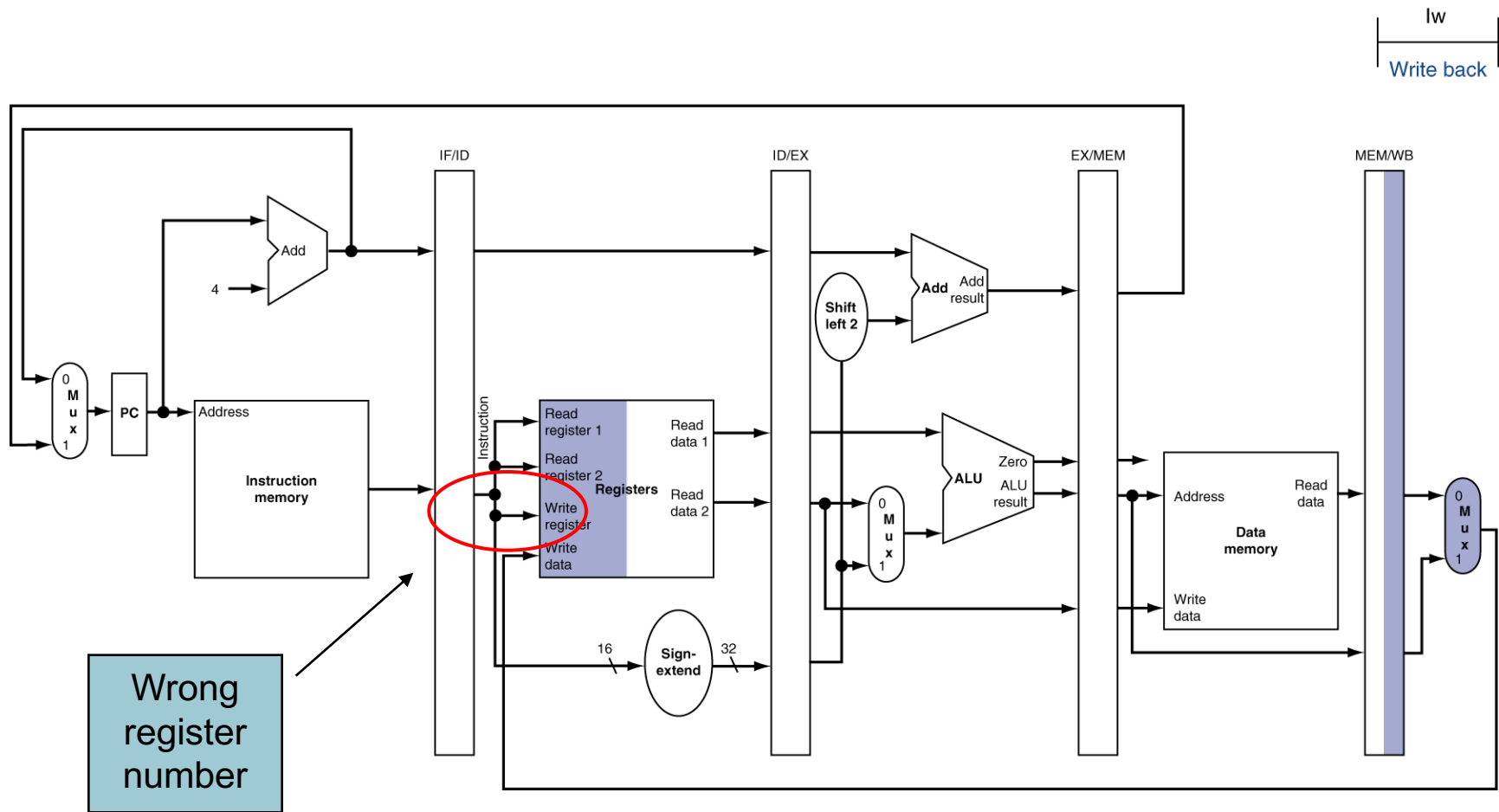


# Corrected Datapath for Load

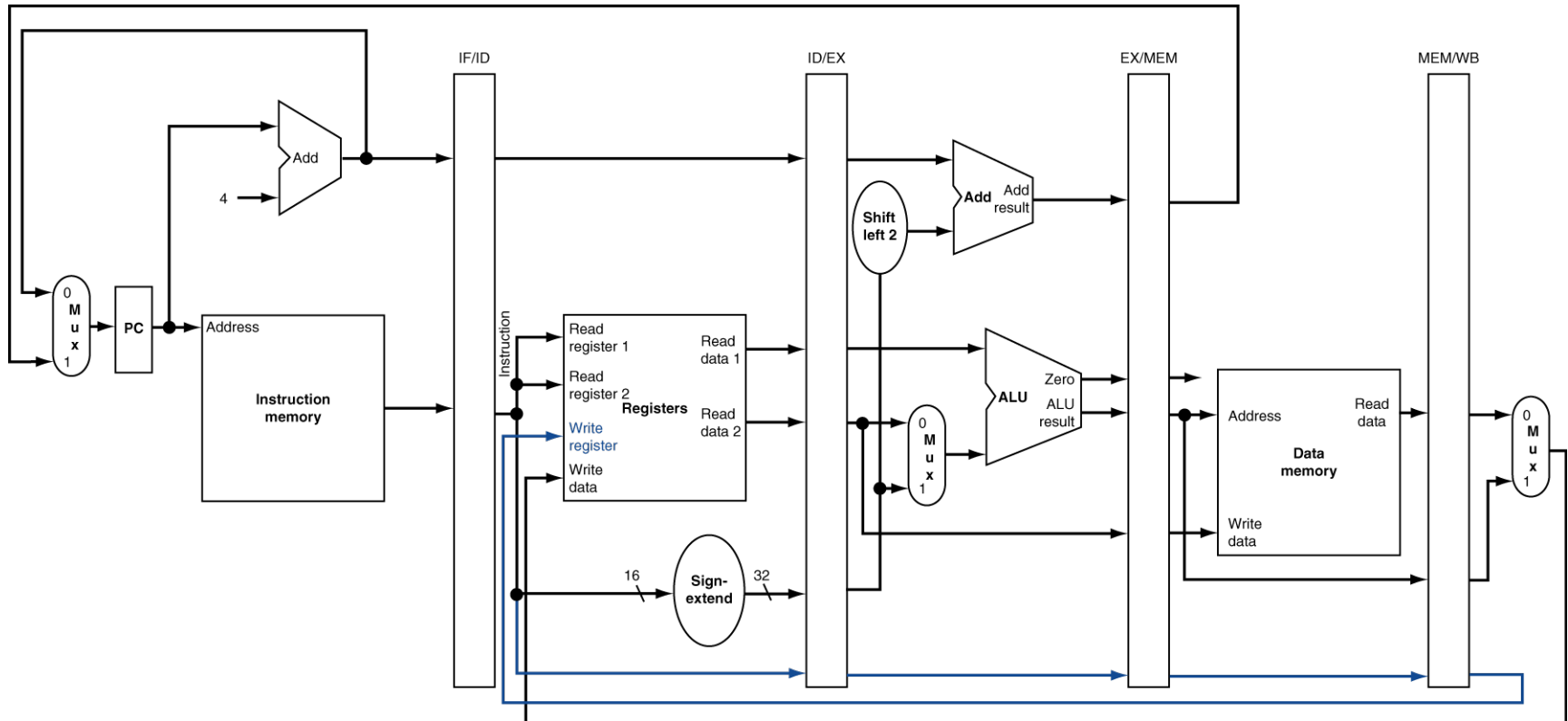


- **Need to preserve the destination register number**
  - Pass the register number from the ID/EX through EX/MEM to the MEM/WB pipeline register for use in the WB stage


# EX for Store

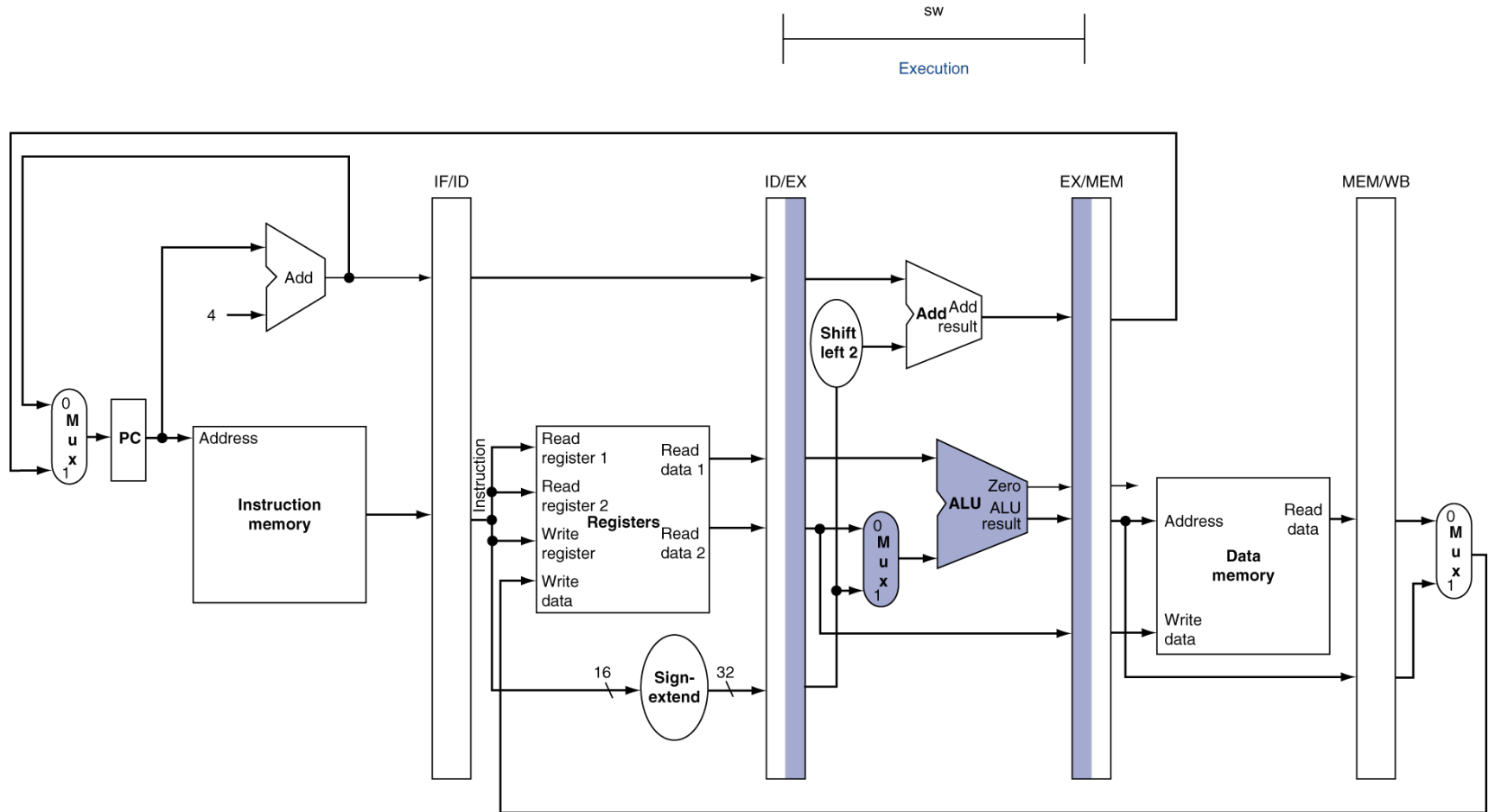

# MEM for Store

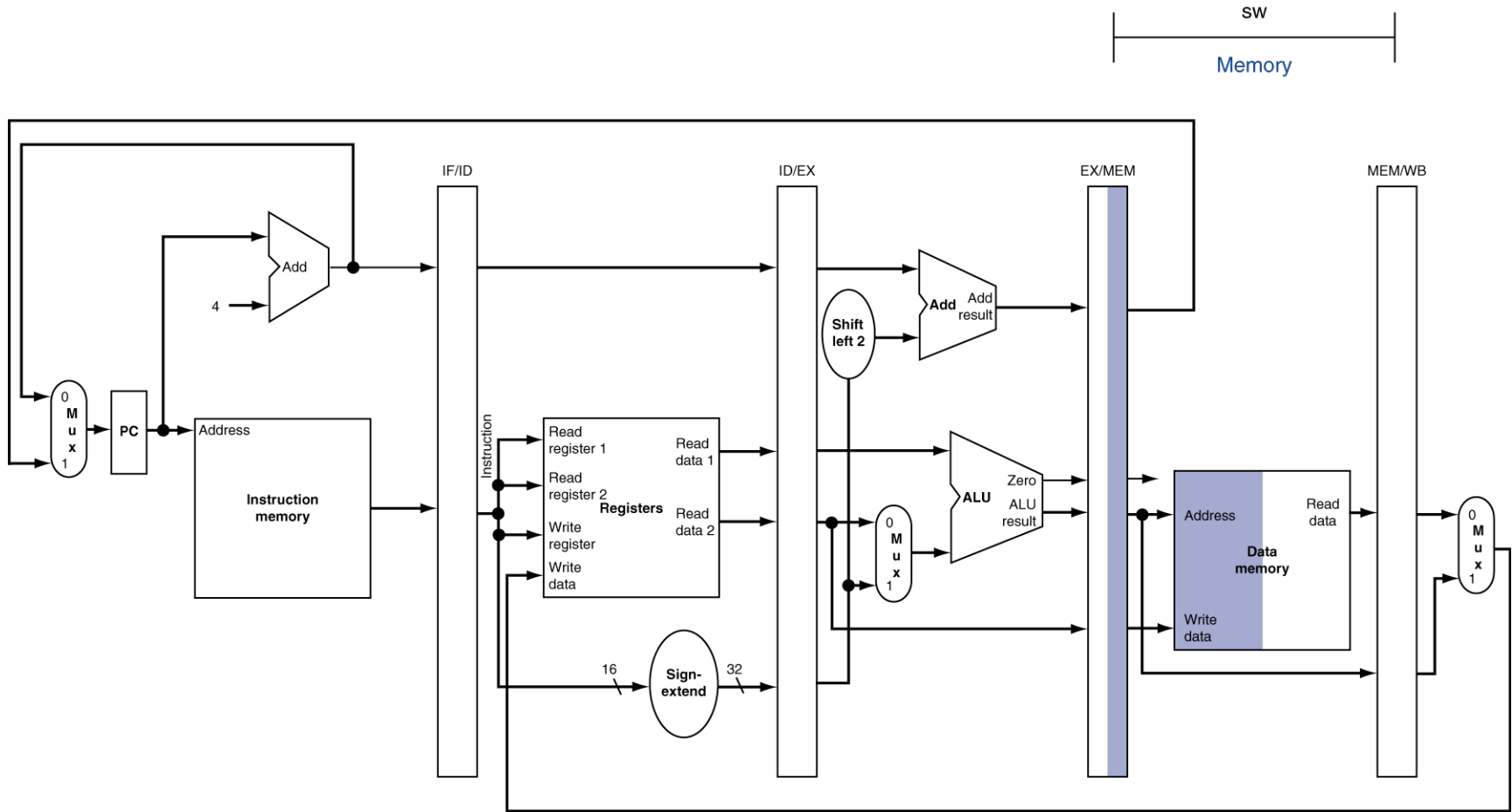

# WB for Store

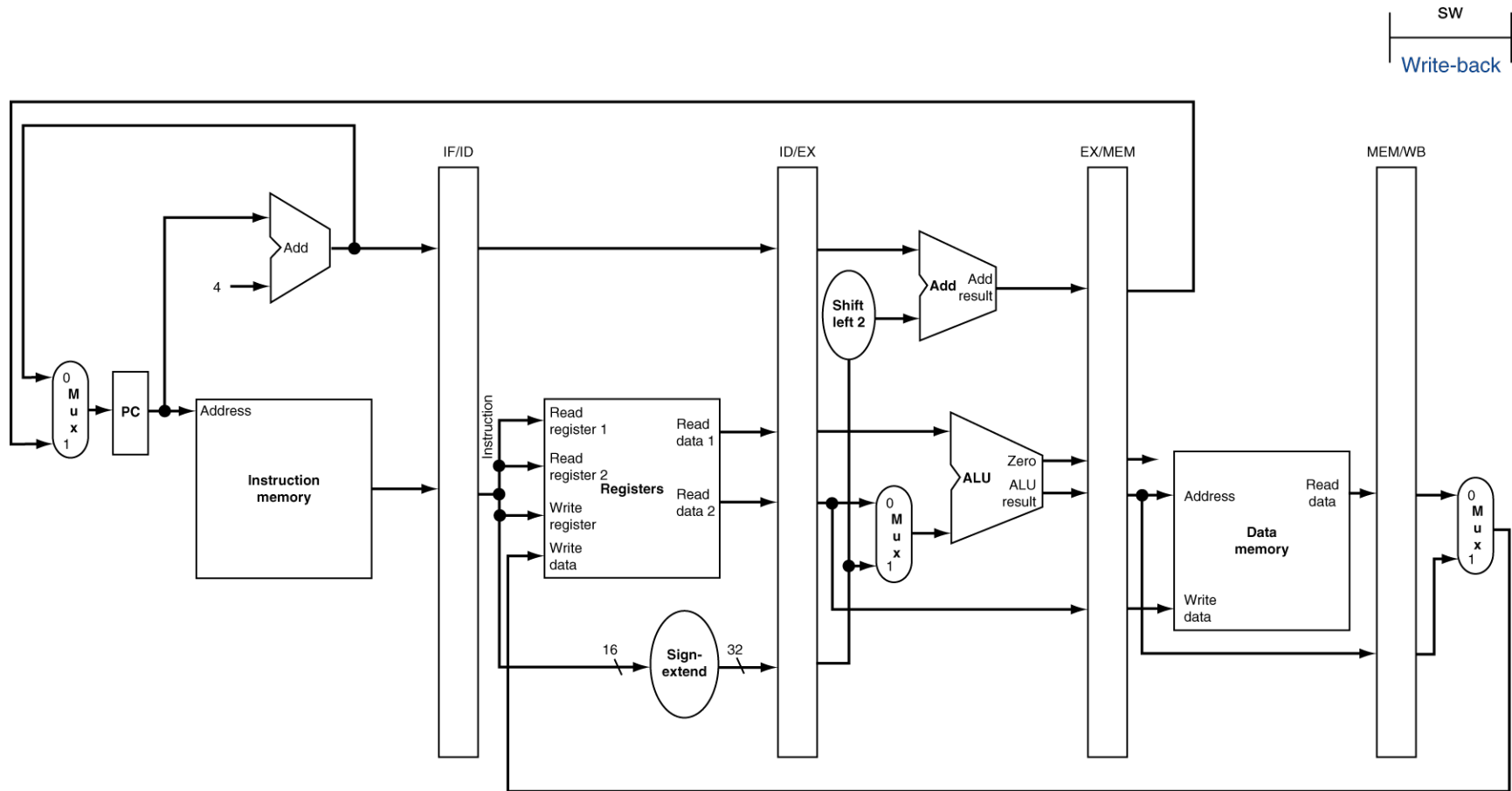

# Multiple instructions

- Consider the following five-instruction sequence:


```
lw    $10, 20($1)
sub    $11, $2, $3
add    $12, $3, $4
lw     $13, 24($1)
add    $14, $5, $6
```

- **Multi-clock-cycle pipeline diagram**
  - Time advances from left to right
  - Program execution advances from the top to the bottom




# Multi-Cycle Pipeline Diagram

## ■ Traditional form

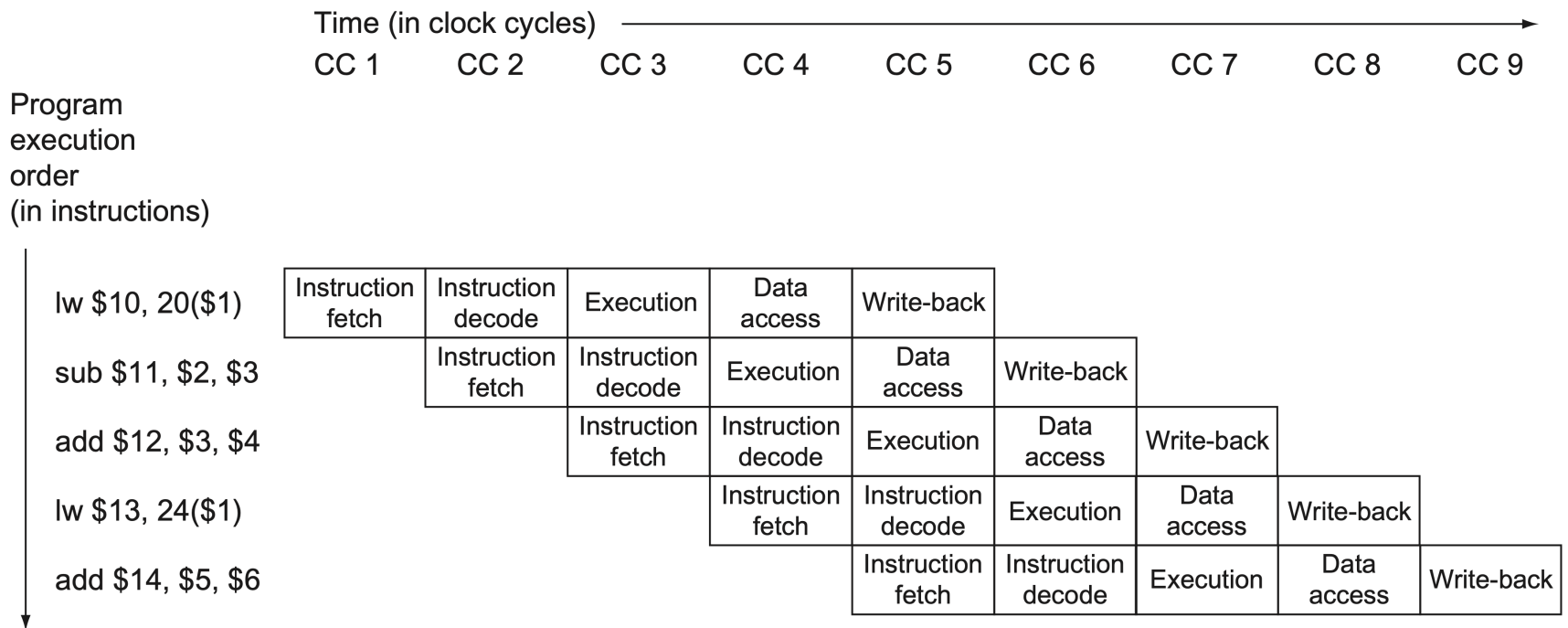


# Multi-Cycle Pipeline Diagram

## ■ Form showing resource usage

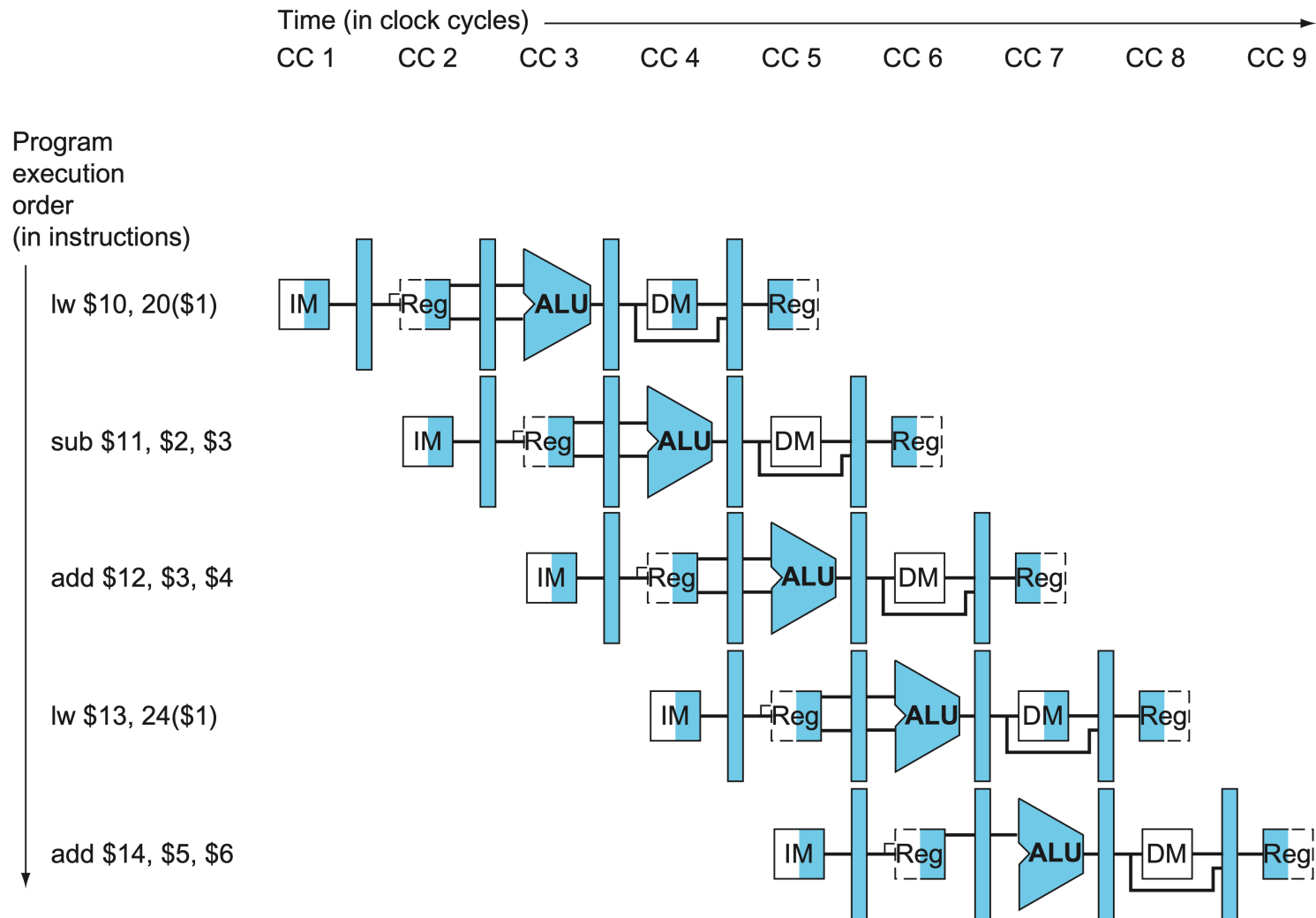

# Single-Cycle Pipeline Diagram (CC5)

add \$14, \$5, \$6	lw \$13, 24 (\$1)	add \$12, \$3, \$4	sub \$11, \$2, \$3	lw \$10, 20(\$1)
Instruction fetch	Instruction decode	Execution	Memory	Write-back

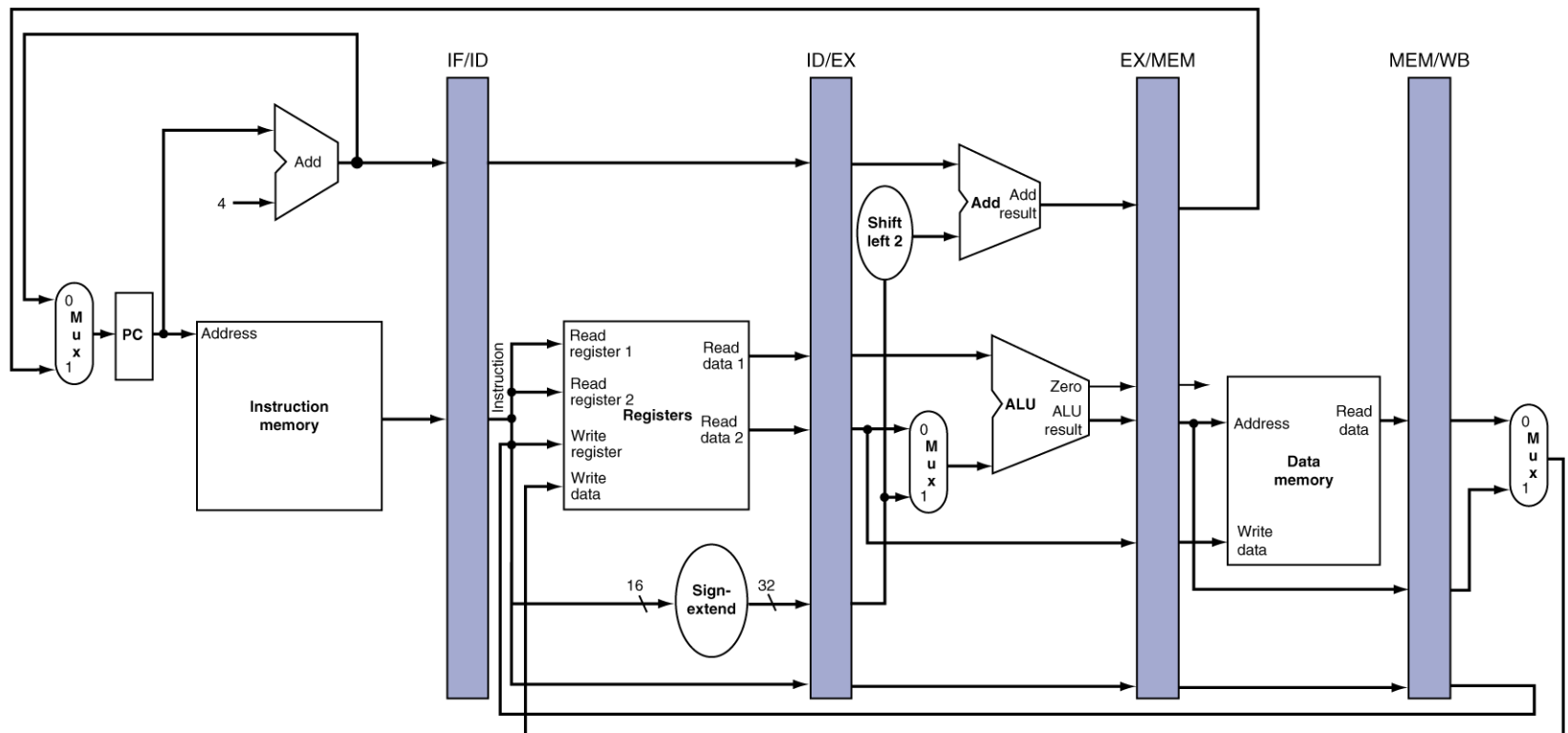

# Pipeline Control Lines

- **We borrow as much as we can from the control for the simple datapath**
  - In particular, we use the same ALU control logic, branch logic, destination-register-number multiplexor, and control lines
- **To specify control for the pipeline, we need only to set the control values during each pipeline stage**
  - No control is required for the IF and ID stages
  - Therefore, we can divide the control lines into three groups according to the pipeline stage

# Pipeline Control Lines


- Set the nine control lines to these values in each stage for each instruction

Instruction	Execution/address calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	RegDst	ALUOp1	ALUOp0	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X


- The simplest way to do this is to **extend the pipeline registers** to include control information
 
# Pipelined Control

- **Control signals derived from instruction**
  - As in single-cycle implementation



# Pipelined Control

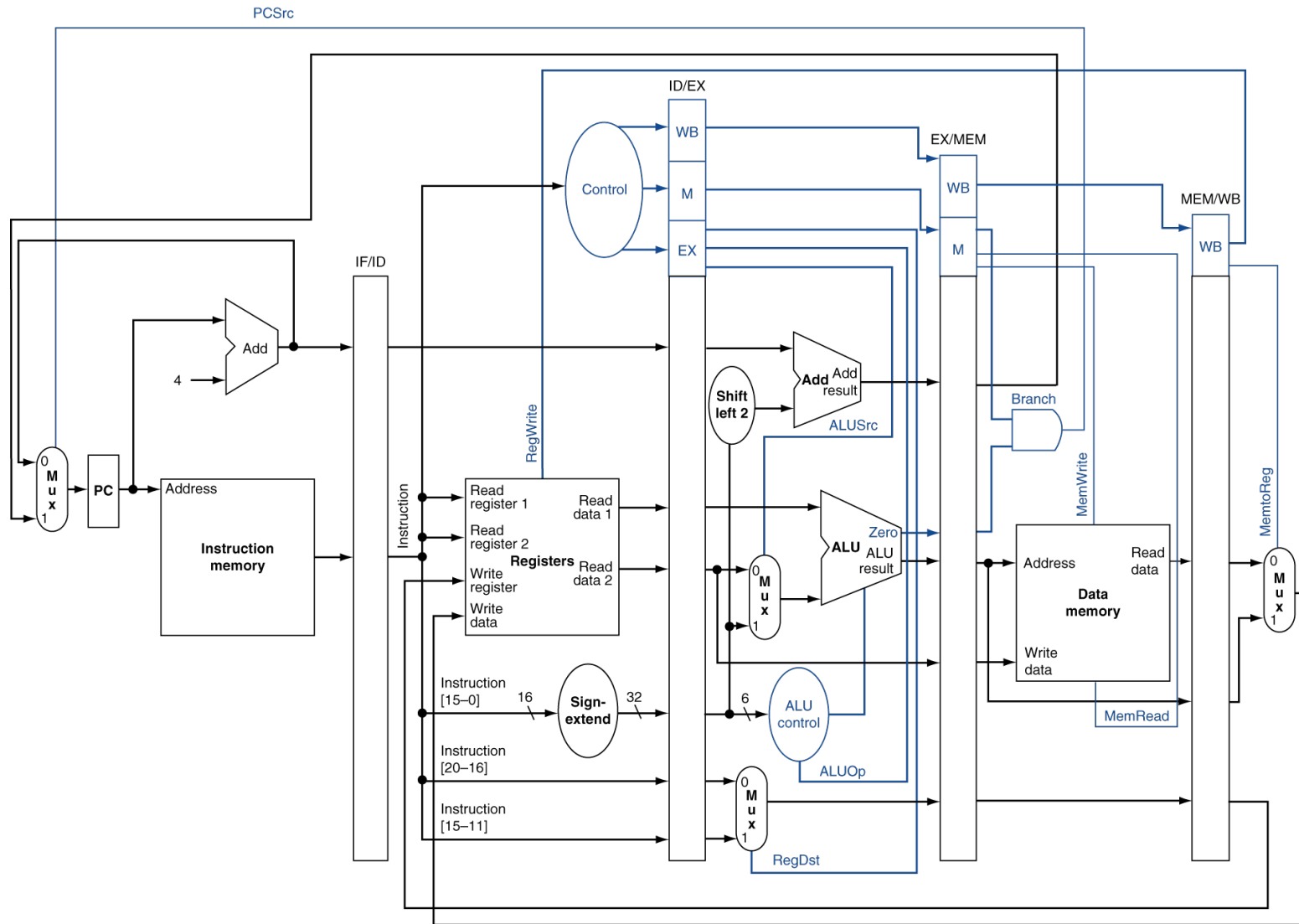

# Pipeline Summary

- **Pipelining improves performance by increasing instruction throughput**
  - Executes multiple instructions in parallel
  - Each instruction has the same latency
- **Instruction set design affects complexity of pipeline implementation**
- **Subject to hazards**
  - Structural, data, control



# Hazards

- **Situations that prevent starting the next instruction in the next cycle**
- **Structural hazards**
  - A required resource is busy
- **Data hazard**
  - Need to wait for previous instruction to complete its data read/write
- **Control hazard**
  - Deciding on control action depends on previous instruction